

1. Calculation (2 points)

1) Obtain the 1s and 2s complements of the following unsigned binary numbers.

00011101

1s:11100010

2s:11100011

2) Perform the indicated subtraction with the following unsigned binary numbers by taking the 2s complement of the subtrahend(减数).

101 – 001000

A:101+111000=111101

| | | |
|---|---|----------------|
| 1 | 0 | I ₂ |
| 1 | 1 | I ₃ |

$$Y = \bar{S}_1\bar{S}_0I_0 + \bar{S}_1S_0I_1 + S_1\bar{S}_0I_2 + S_1S_0I_3$$

2) Please write a verilog description for the circuit by using a process containing case statement.

A:

```
module 1_MUX4T01(S, I, Y);
```

```
input wire [1:0] S;
```

```
input wire [3:0] I;
```

```
output reg      Y;
```

```
always @ (*) begin
```

```
  case (s)
```

```
    2'b00: Y = I[0];
```

```
    2'b01: Y = I[1];
```

```
    2'b10: Y = I[2];
```

```
    2'b11: Y = I[3];
```

```
  endcase
```

```
end
```

```
endmodule
```

endmodule

3) Please write a verilog description for the circuit by using a process containing if- else statement.

A:

```
module 1_MUX4T01(S, I, Y);
input wire [1:0] S;
input wire [3:0] I;
output reg      Y;

always @ (*) begin
    if      (s==2'b00) Y = I[0];
    else if (s==2'b01) Y = I[1];
    else if (s==2'b10) Y = I[2];
    else      Y = I[3];
end
endmodule
```


4) Which function does this circuit accomplish? What is the difference between the circuits implemented by the

two methods in 2) and 3)? (2points)


A: 4-to-1 1bit Multiplexer

circuit in 3) have priorities

正边沿维持阻塞型D触发器

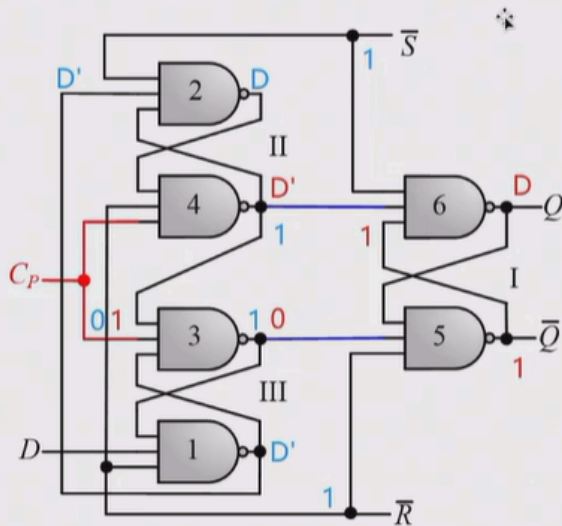


| 异步控制 | | 上升沿触发 | | | |
|----------------|----------------|-------|-----|-----|----------------|
| \overline{R} | \overline{S} | C_p | D | Q | \overline{Q} |
| 0 | 1 | × | × | 0 | 1 |
| 1 | 0 | × | × | 1 | 0 |
| 1 | 1 | ↑ | 0 | 0 | 1 |
| 1 | 1 | ↑ | 1 | 1 | 0 |

 

4. Analysis states (10 points)


Please draw the state diagram of "101" sequential detector (simplified as far as possible) and the input、output as following:

(1) Input A: 0 1 0 1 | 0 1 1 0 1
Output Z: 0 0 0 1 0 1 0 0 1

 

(2) Input A: 0101011010
Output Z: 0001000010

A:

 



5. Sequential Circuits analysis (20 points)

1) A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z. The state table following:

| Present state | | Inputs | | Next state | | Output |
|---------------|----------|----------|----------|------------|----------|----------|
| <i>A</i> | <i>B</i> | <i>X</i> | <i>Y</i> | <i>A</i> | <i>B</i> | <i>Z</i> |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 |

 (c) it has an inertial delay of 0.06 ns with a reject time of 0.06 ns. (10 points)



 



2. Find the delay from each input to the output.

(a) Finding t_{PHL} and t_{PLH} for each path, assuming $t_{PHL} = 0.30\text{ns}$ and $t_{PLH} = 0.50\text{ns}$ for each gate. From these values, find t_{pd} for each path.

(b) Using $t_{pd} = 0.40\text{ns}$ for each gate.

 (c) Compare your answers in (a) and (b) and discuss the differences. (10 points)



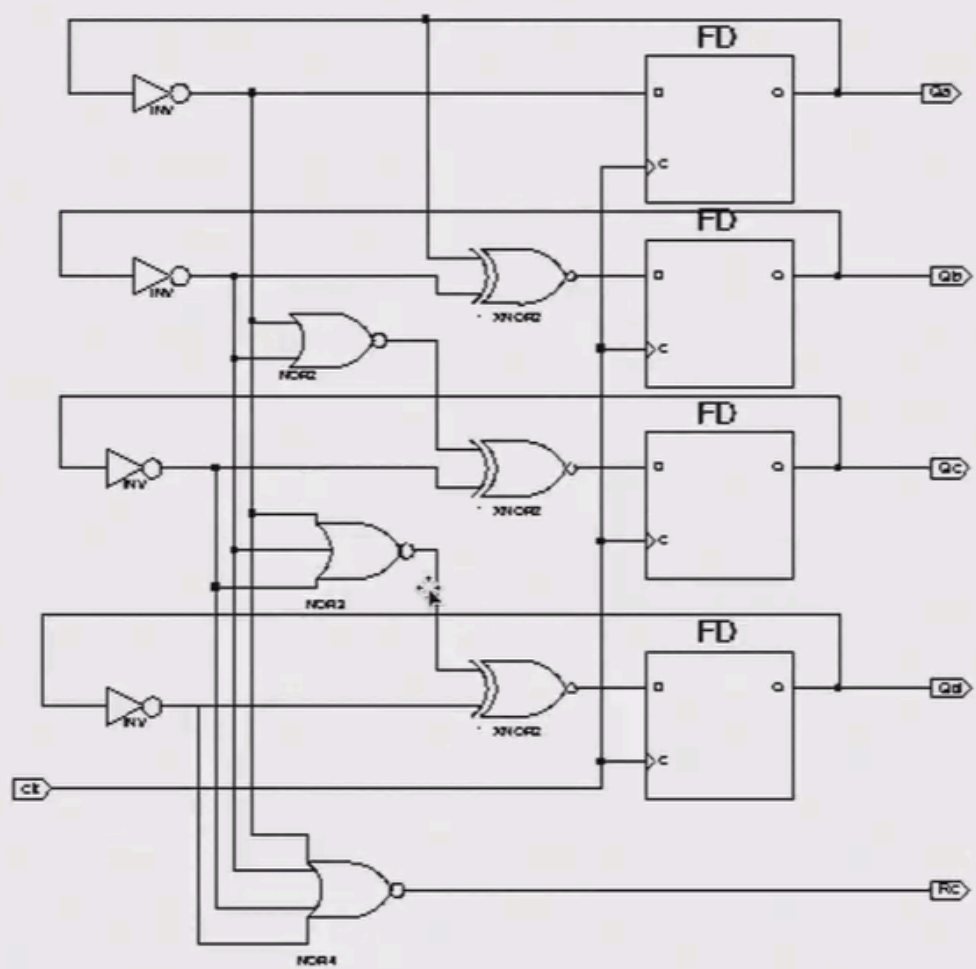

(a) Please write the state table.

| | Q_A | Q_B | Q_C | Q_D | D_A | D_B | D_C | D_D |
|---|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 2 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 3 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 4 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 5 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 6 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| 7 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 8 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |